

# A Brighter Flicker Candle - Matthew D. Jordan

R1 = 2 @ 100ohm 1/2watt Resistor

R2 = 4 @ 47ohm 1/2watt Resistor

M1 = 4 @ IRF510A Mosfet (or similar)

LED = 4 @ 3.2v (RL8-W110-360 from superbrightleds.com)

